

DATE

EXP NO: 6

# VERIFICATION OF MAXIMUM POWER TRANSFER THEOREM

AIM:

To measure the power absorbed in a load and to verify that the power absorbed in a load is maximum only when load resistance is equal to the source resistance.


APPARATUS REQUIRED:

SNO	NAME OF APPARATUS	RANGE/ RATING	QUANTITY
1	Voltmeter	(0-15) M $\Omega$	1
2	Ammeter	(0-500) mA M $\Omega$	1
3	Resistor	560 $\Omega$ , 470 $\Omega$	2, 1
4	RPS [DC supply]	15 V	1

PROCEDURE:

1. Make connections as per the circuit diagram.
2. Change the resistors  $R_L$  whose value close to  $R_{TH}$ , measure the corresponding  $V_L$ ,  $I_L$  and calculate the power  $P_L$  and enter into the table (2).
3. Plot a graph between  $R_L$  and  $P_L$  and find the  $R_L$  corresponding to maximum power transfer.
4. Verify the measured values of  $R_L$  at maximum power transfer as same as calculated and found graphically.

### CIRCUIT DIAGRAM:

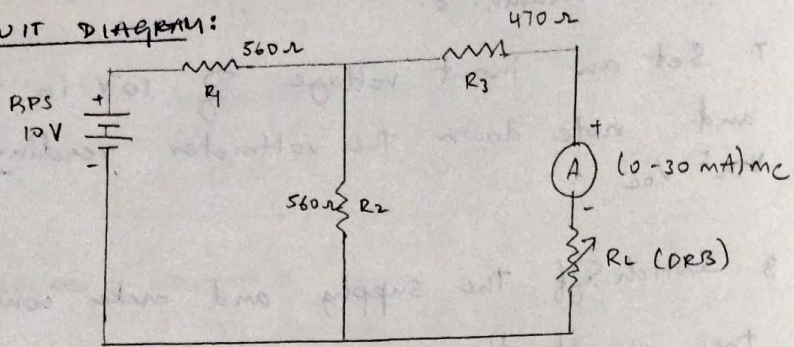

### MODEL GRAPH:

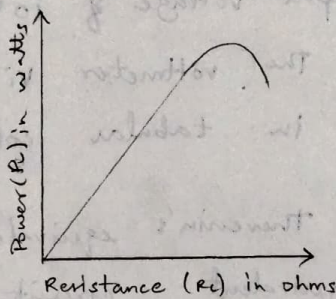


TABLE (i): FOR PRACTICAL CALCULATION:

Sno	Load Resistance ( $R_L$ ) in ohm.	Load current ( $I_L$ ) in mA	Load voltage ( $V_L$ ) in volts	Load power in watts.
1	1 kΩ	2.96 mA	2.96 V	8.76 mW
2	150 Ω	5.53 mA	0.995 V	5.504 mW
3	100 kΩ	6.00 mA	0.6 V	3.6 mW
4	470 Ω	4.13 mA	1.94 V	8.01 mW
5	5.1 Ω	0.85 mA	4.335 V	3.684 mW

### CALCULATION:

$$V_{TH} = \frac{V \times R_2}{R_1 + R_2} = \frac{10 \times 500}{2(560)} = 5V$$

$$R_{TH} = \frac{560 \times 560}{2(560)} + 470 \Rightarrow 280 + 470 = 750 \Omega$$

$$\therefore R_L = R_{TH}$$

$$P_L = \frac{(V_{TH})^2}{4(R_{TH})} = \frac{(5)^2}{4 \times 750} = \frac{25}{3000} = 0.0083W$$

$$= 8.38 mW$$



RESULT:

Thus Maximum Power transfer theorem is verified practically and theoretically.



$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{5}{1500} = 0.00333 A$$

$$I_L = 3.33 \text{ mA}$$

$$V_L = I_L \times R_L$$

$$= 3.33 \times 10^{-3} \times 750$$

$$\boxed{V_L = 2.5 \text{ V}}$$

S. No.	Name of Apparatus	Quantity
1	Voltmeter	(0-12) V
2	Ammeter	(0-200) mA
3	Resistor	250 $\Omega$ , 750 $\Omega$
4	DC Supply	12 V

PROCEDURE

1. Make connections as per the circuit diagram.
2. Change the resistance R, whose value close to  $R_{Th}$ , measure the corresponding  $V_L$  and  $I_L$  and calculate the power P and enter into the table (2).
3. Plot a graph between P and R and find the maximum power transfer.